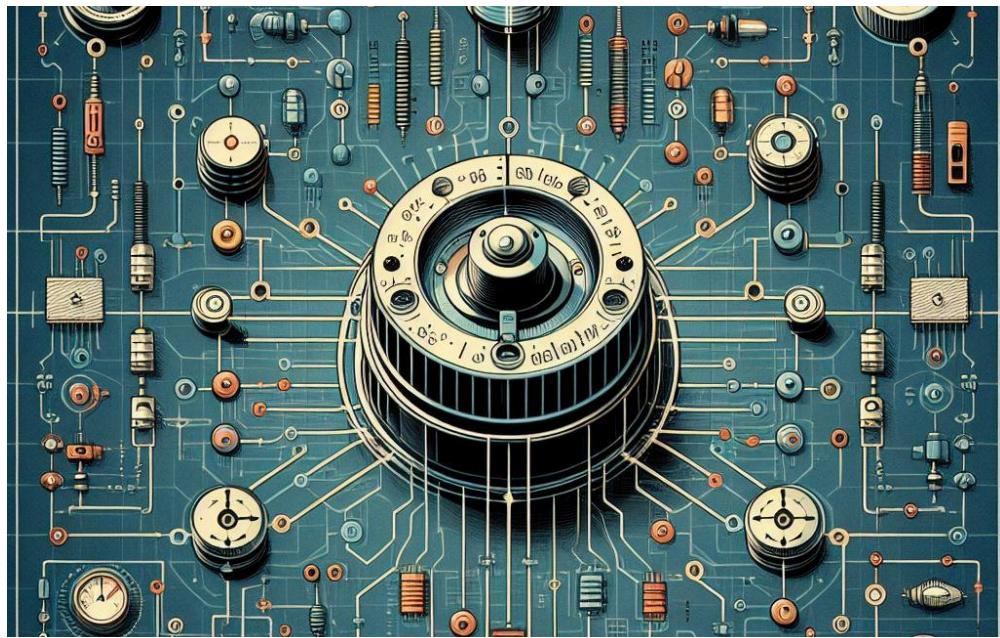


Post Lab Report of Electrical Circuits

Lab 02: Series-Parallel DC Circuit and Verification of Kirchhoff's Laws



Submitted By: Group 2

Akhlaq Hossain

2022-3-60-057

<https://ahjim.com>

Saba Tasnim Khan

2022-3-60-049

Momo Bhuiyan

2022-2-60-020

Sabiha Nusrat

2022-1-60-303

Submitted To:

M. Saddam Hossain Khan

Senior Lecturer

Department of CSE

East West University

Post Lab Report

Question 1: Calculate the values of V₁, V₂, V₃, I₁, I₂, and I₃ of the circuit using measured values of E, R₁, R₂, and R₃. Compare the calculated values with the measured values and give reason if any discrepancy is found.

Solution:

We know,

$$R_p = 1 / (1 / 46.8 + 1 / 98.9) = 31.767\Omega$$

So,

$$R_{eq} = 100.2 + 31.767 = 131.97\Omega$$

So,

$$I_1 = E / R_{eq} = 3 / 131.97 = 0.023A$$

Now,

$$V_1 = I_1 * R_1 = 0.023 * 100.2 = 2.28V$$

$$V_2 = I_1 * R_p = 0.023 * 31.767 = 0.72V$$

$$V_3 = I_1 * R_p = 0.023 * 31.767 = 0.72V$$

$$I_2 = V_2 / R_2 = 0.72 / 46.8 = 0.015A$$

$$I_3 = V_3 / R_3 = 0.72 / 98.9 = 0.007A$$

Title	Measured Values	Calculated values
Value of E (V)	3	3
Value of V ₁ (V)	2.2	2.28
Value of V ₂ (V)	0.8	0.72
Value of V ₃ (V)	0.8	0.72
Value of I ₁ (mA)	20	23
Value of I ₂ (mA)	13	15
Value of I ₃ (mA)	6	7

The discrepancy is mainly because of mechanical and Human errors.

Question 2: From the calculated values of V_1 , V_2 , V_3 , I_1 , I_2 , and I_3 , show that (i) $V_2 = V_3$, (ii) $E = V_1 + V_2$ (KVL), and (iii) $I_1 = I_2 + I_3$ (KCL).

Solution:

(i) From the calculated values of V_2 and V_3 , We see,

$$V_2 = V_3 = 0.72V$$

(ii) From the calculated values,

$$V_1 = 2.28V$$

$$V_2 = 0.72V \quad \text{and}$$

$$E = 3V$$

So,

$$V_1 + V_2 = 2.28 + 0.72 = 3V = E$$

(iii) From the calculated values,

$$I_1 = 23mA$$

$$I_2 = 15mA \quad \text{and}$$

$$I_3 = 7mA$$

So,

$$I_2 + I_3 = 15 + 7 = 22mA \approx I_1$$

-----x-----

Group :02

Members: 1) Akhlaq Hossain (2022-3-60-057)

- 2) Saba Tasnim (2022-3-60-049)
- 3) Momo Bhuiyan (2022-2-60-020)
- 4) Sabika Nasrat (2022-1-60-303)

Lab:2 (Series-Parallel DC Circuit & verification of Kirchhoff's Law.)

Measured value of E (V)	Measured value of V_1 (V)	Measured value of V_2 (V)	Measured value of V_3 (V)	Measured value of I_1 (mA)	Measured value of I_2 (mA)	Measured value of I_3 (mA)	Measured value of Resistances (Ω)
3	2.2	0.8	0.8	20	13	6	$R_1 = 100.2$ $R_2 = 46.8$ $R_3 = 98.9$

Lab procedure:-

3.

(i) We got,

$$V_2 = 0.8 \text{ V}$$

$$V_3 = 0.8 \text{ V}$$

$$\therefore V_2 = V_3$$

~~DATA~~
20/2/24

(ii) We got, $V_1 = 2.2 \text{ V}$

$$V_2 = 0.8 \text{ V}$$

$$\therefore V_1 + V_2 = (2.2 + 0.8) \text{ V} = 3 \text{ V}$$

$$\therefore E = 3 \text{ V}$$

(iii) We got, $I_1 = 20 \text{ mA}$; $I_2 = 13 \text{ mA}$ & $I_3 = 6 \text{ mA}$

$$\therefore I_2 + I_3 = (13 + 6) \text{ mA} = 19 \text{ mA}$$

$$\therefore I_1 = I_2 + I_3$$

$$\therefore I_1 \approx I_2 + I_3$$

Aklhale Hossain

2022-3-60-057

CSE203-Lab-2

Section: 4

Group: 2

Pre Lab (2)

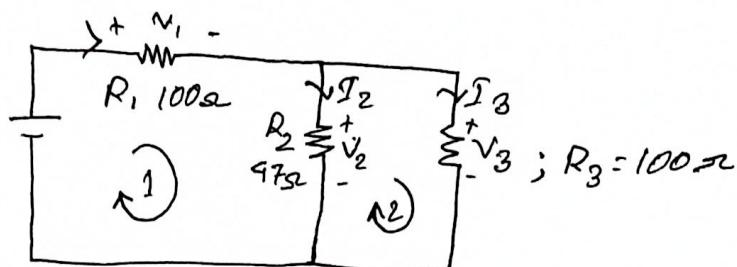


Figure: Circuit for Experiment

Solution:

Applying KVL at loop 1:

$$3 - V_1 - V_2 = 0$$

$$\Rightarrow 3 - 100I_1 - 47I_2 = 0 \quad \dots \textcircled{1}$$

Applying KVL at loop 2:

$$V_3 + V_2 = 0$$

$$\Rightarrow 47I_2 + 100I_3 = 0 \quad \dots \textcircled{11}$$

Applying KCL at node a, $I_1 = I_2 + I_3 \quad \dots \textcircled{111}$

Solving eqn ①, ⑪ and ⑬ we get,

$$3 - 100(I_2 + I_3) - 47I_2 = 0$$

$$\Rightarrow 3 - 147I_2 - 100I_3 = 0$$

$$\therefore I_1 = 0.23A \quad \text{and} \quad V_1 = 2.3V$$

$$I_2 = 0.159A \quad V_2 = 0.723V$$

$$I_3 = 0.0072A \quad V_3 = 0.723V$$

Answer 2:

we got,

(1)

$$V_2 = 0.723V; V_3 = 0.723V, *$$

$$\therefore V_2 = V_3$$

(II)

we got,

$$V_1 = 2.3V; V_2 = 0.723V$$

$$\therefore V_1 + V_2 = (2.3 + 0.723)$$

$$= 3.023 \checkmark$$

$$\approx 3V$$

$$\therefore E = 3V$$

$$\therefore V_1 + V_2 = E$$

(III)

we got,

$$I_1 = 0.23A, I_2 = 0.159A \text{ and } I_3 = 0.0072A$$

$$\therefore I_2 + I_3 = (0.159 + 0.0072)A = 2.3A = I_1$$

$$\therefore I_1 = I_2 + I_3$$

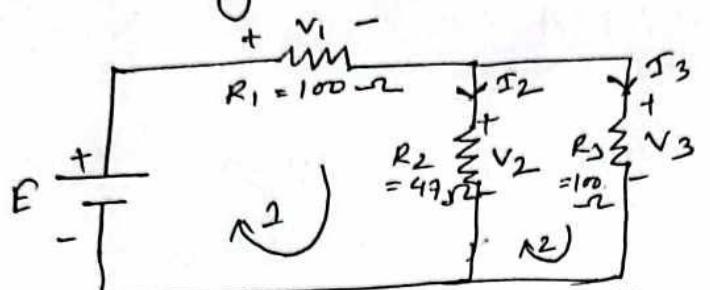
Pre-lab-2Circuit Diagram:-

Fig: Circuit for Experiment

Soln:-

Applying KVL at loop 1,

$$3 - V_1 - V_2 = 0$$

$$\Rightarrow 3 - 100I_1 - 47I_2 = 0 \dots \textcircled{1}$$

Applying KVL at loop 2-

$$V_2 + V_3 = 0$$

$$\Rightarrow 47I_2 + 100I_3 = 0 \dots \textcircled{11}$$

Applying KCL at node a, $I_1 = I_2 + I_3 \dots \textcircled{111}$ Solving eq'n $\textcircled{1}$, $\textcircled{11}$ and $\textcircled{111}$ we get,

$$3 - 100(I_2 + I_3) - 47I_2 = 0$$

$$\Rightarrow 3 - 147I_2 - 100I_3 = 0$$

$$\therefore I_1 = 0.23A \quad \text{and,} \quad V_1 = 2.3V$$

$$I_2 = 0.154A \quad V_2 = 0.723V$$

$$I_3 = 0.0072A \quad V_3 = 0.723V$$

② (ii) We got, $V_2 = 0.723V$
 $V_3 = 0.723V$

$$\therefore V_2 = V_3$$

(iii) We got, $V_1 = 2.3V$
 $V_2 = 0.723V$

$$\therefore V_1 + V_2 = (2.3 + 0.723)V$$

$$= 3.023V$$

$$\approx 3V$$

$$\therefore E = 3V$$

$$\therefore V_1 + V_2 = E$$

(iii) We got, $I_1 = 0.23A$, $I_2 = 0.154A$
 ad $I_3 = 0.0072A$

$$\therefore I_2 + I_3 = (0.154 + 0.0072)A$$

$$= 0.1612A$$

$$= I_1$$

$$\therefore I_1 = I_2 + I_3$$

∴ Solution:

From figure 4,

$$R_x = R_2 \parallel R_3$$

$$\Rightarrow \frac{1}{R_x} = \left(\frac{1}{47} + \frac{1}{100} \right)$$

$$\Rightarrow R_x = \left(\frac{1}{47} + \frac{1}{100} \right)^{-1}$$

$$= 31.97 \Omega$$

$$R_{eq} = R_1 + R_x$$

$$= 100 + 31.97 \Omega$$

$$= 131.97 \Omega$$

We know that,

$$E = I_1 R_{eq}$$

$$I_1 = \frac{3}{131.97} = 0.02273243919 A \times 10^{-3}$$

$$= 22.7 mA$$

$$I_2 = \frac{R_3 \times I_1}{R_2 + R_3}$$

$$= \frac{100 \times 22.7}{47 + 100}$$

$$= 15.44 mA$$

minimum deviation and prism angle?

$$I_3 = \frac{R_2 * I_1}{R_2 + R_3}$$

$$= \frac{47 \times 22.7}{47 + 100}$$

$$= 7.26 \text{ mA}$$

Applying Ohm's law,

$$V_1 = I_1 R_1 = (22.7 \text{ mA} \times 100 \Omega) = 2.27 \text{ V}$$

$$V_2 = I_2 R_2 = (15.44 \text{ mA} \times 47 \Omega) = 0.72 \text{ V}$$

$$V_3 = I_3 R_3 = (7.26 \text{ mA} \times 100 \Omega) = 0.72 \text{ V}$$

2. Solution:

From question no. 1

$$I_1 = 22.7 \text{ mA}, I_2 = 15.44 \text{ mA}, I_3 = 7.26 \text{ mA}$$

$$V_1 = 2.27 \text{ V}, V_2 = 0.72 \text{ V}, V_3 = 0.72 \text{ V}$$

(i) Here, the value of V_2 and V_3 are equal.
Their values should be same, because
the voltages of parallel circuit are always
equal.

$$\therefore V_2 = V_3 \text{ (Shown)}$$

(ii) From question 1,

$$V_1 = 2.27 V, V_2 = 0.72 V$$

Using KVL at loop 1,

$$\begin{aligned} E &= V_1 + V_2 \\ &= (2.27 + 0.72) V \\ &= 3 V \end{aligned}$$

(iii) From question 1,

$$I_1 = 22.7 \text{ mA}$$

$$I_2 = 15.44 \text{ mA}$$

$$I_3 = 7.26 \text{ mA}$$

Using KCL at node 2,

~~I₂~~

$$-I_1 + I_2 + I_3 = 0$$

$$\Rightarrow I_1 = I_2 + I_3$$

$$-(15.44 \text{ mA} + 7.26 \text{ mA})$$

$$= 22.7 \text{ mA}$$

Name : Sabiha Nusrat

ID : 2022-1-60-303

CSE 209 : Electric Circuit

Section : 04

Pre lab Report : 02

Lab Expt No : 2

Title :- Series- Parallel DC Circuit and Verification

of Kirchhoff's laws.

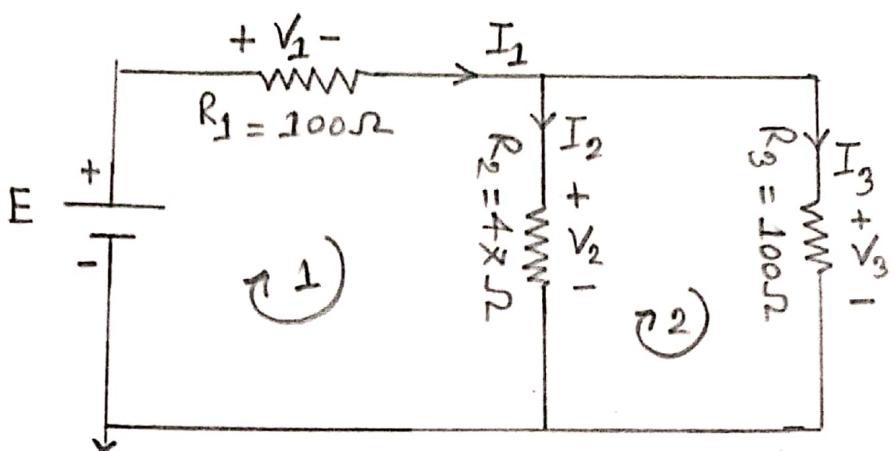


Figure 4. Circuit for experiment.

Pre Lab Question Answer:-

Applying KVL at loop 1;

$$3 - V_1 - V_2 = 0$$

$$\Rightarrow 3 - 100I_1 - 4 \times I_2 = 0 \dots \dots \textcircled{i}$$

Applying KVL at loop 2, $V_2 + V_3 = 0$

$$\Rightarrow 4 \times I_2 + 100I_3 = 0 \dots \dots \textcircled{ii}$$

Applying KCL at node a, $I_1 = I_2 + I_3 \dots \dots \textcircled{iii}$

Solving equation \textcircled{i} , \textcircled{ii} & \textcircled{iii} , we get;

$$3 - 100(I_2 + I_3) - 4 \times I_2 = 0$$

$$\Rightarrow 3 - 14 \times I_2 - 100I_3 = 0$$

$$\therefore I_1 = 0.23A \quad \& \quad V_1 = 2.3V$$

$$I_2 = 0.134 A$$

$$V_2 = 0.723 V$$

$$I_3 = 0.0072 A$$

$$V_3 = 0.723 V$$

② \Rightarrow

(i) We got $V_2 = 0.723 V$

$$V_3 = 0.723 V$$

$$\therefore V_2 = V_3$$

(ii) We got, $V_1 = 2.3 V$

$$V_2 = 0.723 V$$

$$\therefore V_1 + V_2 = (2.3 V + 0.723 V)$$

$$= 3.023 V$$

$$\therefore E \approx 3 V$$

$$\therefore V_1 + V_2 = E$$

(iii) We got, $I_1 = 0.23 A$, $I_2 = 0.154 A$

$$\& I_3 = 0.0072 A$$

$$\therefore I_2 + I_3 = (0.154 + 0.0072) A$$

$$= 0.23 A$$

$$= I_1$$

$$\therefore I_1 = I_2 + I_3$$